

1278**Code : 15EE-21T**Register
Number

--	--	--	--	--	--	--

II Semester Diploma Examination, Nov./Dec. 2016**ELECTRICAL CIRCUITS****Time : 3 Hours]****[Max. Marks : 100**

- Note :** (i) Answer any **six** questions from Part – A. Each question carries **5** marks.
(ii) Answer any **seven** questions from Part – B. Each question carries **10** marks.

PART – A

1. Explain : **5**
 - (i) Closed Circuit
 - (ii) Open CircuitWith neat circuit diagrams
2. State Kirchoff's voltage law. With a neat circuit diagram, write the equation for Kirchoff's voltage law. **5**
3. Define the followings with SI units : **5**
 - (i) Magnetic flux
 - (ii) Flux density
 - (iii) Absolute permeability
 - (iv) Relative permeability
 - (v) Reluctance
4. State and explain Fleming's right hand thumb rule. **5**
5. Write a sinusoidal wave form and mark **5**
 - (i) Maximum value
 - (ii) Time period
 - (iii) Cycle
 - (iv) Instantaneous value
6. Compute an equation for RMS value of an alternating current. **5**

7. Explain with a neat circuit diagram, a pure resistive circuit and write its

- (i) Waveform
- (ii) Vector diagram
- (iii) Power consumption

5

8. Define resonance and explain condition for series resonance.

5

9. Show that line voltage = $\sqrt{3}$ phase voltage in 3- ϕ star connected system.

5

PART - B


10. (a) Define :

4

- (i) Active circuit
- (ii) Passive circuit

(b) Calculate magnitude and show the direction of current through the battery for the given circuit by applying Kirchoff's laws

6

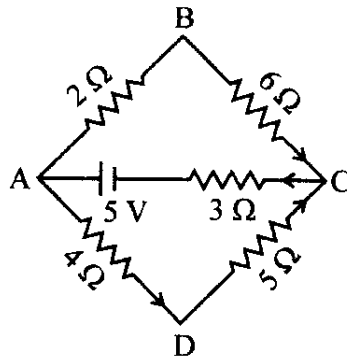


11. (a) State and explain super position theorem.

4


(b) Calculate the total resistance and current for the circuit given below using star-delta transformation

6

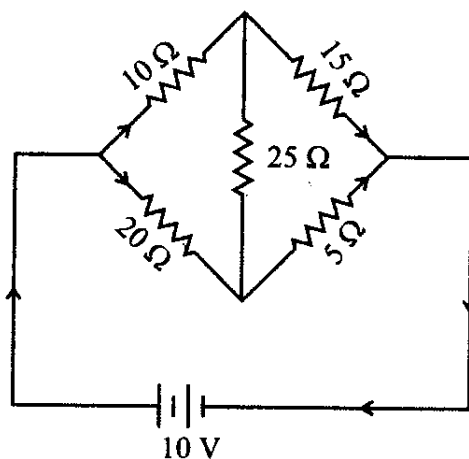

12. (a) Apply reciprocity theorem for the circuit given below :

6

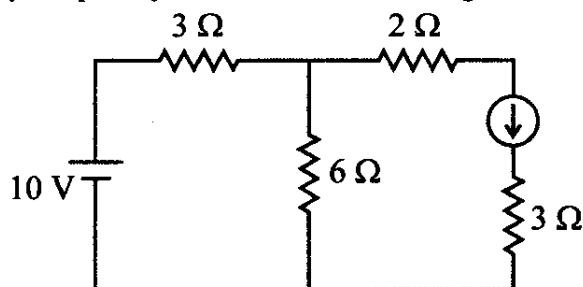

- (b) Define :
- (i) Linear circuit
- (ii) Unilateral circuit
13. (a) Compare magnetic circuit with electric circuit. 5
- (b) An air-cored coil has 3000 turns and carries a current of 0.12 amps. The cross sectional area of the coil is 5 cm^2 and length of magnetic circuit is 18 cm, find the
- (i) Magnetic field strength
- (ii) Flux density
- (iii) Total flux in the coil 5
14. (a) Compute an expression for energy stored in a magnetic field. 5
- (b) A coil of 70 cm length and 2.5 sq cm area of cross section has 1000 turns on it. Calculate inductance of the coil when
- (i) The core is air core
- (ii) The core is iron core of $\mu_r = 1000$ 5
15. (a) Define : 5
- (i) Self Inductance
- (ii) Faraday's laws of electromagnetic induction
- (b) Define the followings : 5
- (i) RMS value
- (ii) Average value

[Turn over

16. (a) Compute an equation for instantaneous value of an voltage and current. 4
(b) A sinusoidal alternating current is represented by $i = 120 \sin 377 t$.
Calculate :
(i) Maximum value
(ii) Current when $t = 0.002$ sec passing through zero in +ve direction.
(iii) RMS value of current 6
17. (a) Two vectors are given in rectangular form $I_1 = 2 + i3$ and $I_2 = 5 + i6$. Calculate : 5
(i) $I_1 + I_2$
(ii) $I_1 \times I_2$
(b) Explain with diagram R-L series circuit and compute an equation for power consumption. 5
18. (a) Define the following : 5
(i) Impedance (Z)
(ii) Capacitive reactance (X_C)
(iii) Inductive reactance (X_L)
(b) A circuit consists of resistance 20Ω and an inductance of 0.3 h 5
Calculate :
(i) Inductive reactance (X_L)
(ii) Impedance of circuit (Z) at 50 Hz frequency
19. (a) A resistance of 10Ω , an inductive reactance of 30Ω and capacitive reactance of 60Ω are connected in series across 200 V , 50 Hz supply. Calculate : 5
(i) Impedance
(ii) Current taken
(iii) Voltage a/c each element
(iv) P.f. of the circuit
(b) Explain with diagram two watt meter method of measurement of 3- ϕ power. 5