

1458**Code : 15EE-21T**

Register
Number

--	--	--	--	--	--	--

II Semester Diploma Examination, April/May-2016**ELECTRICAL CIRCUITS****Time : 3 Hours]****[Max. Marks : 100**


- Note :** (i) Answer any **Six** questions from Part-A. Each questions carries **5** marks.
(ii) Answer any **Seven** questions from Part-B. Each full questions carries **10** marks.

PART - A


1. Define Node, Linear circuit and Active circuit. **5**
2. List and explain the electrical circuit elements. **5**
3. Define : (i) flux (ii) reluctance, Write their units. **5**
4. State and explain Faraday's laws of electromagnetic induction. **5**
5. Explain the mid-ordinate method of calculating the RMS. Value of an alternating voltage and current. **5**
6. Draw the sinusoidal waveform and mark peak value, time period & cycle of an alternating quantity. **5**
7. Draw the circuit diagrams waveform and vector diagram for pure inductive circuit. **5**
8. Define :
(i) leading power factor
(ii) lagging power factor
(iii) unity power factor
With vector diagram **5**
9. Write the relationship between line voltage, line current, phase voltage, phase current in three phase star and delta connected system, with circuit diagram. **5**

PART - B

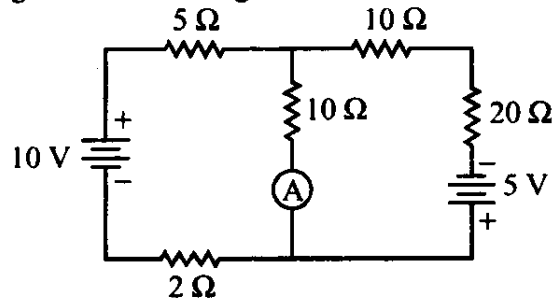
10. (a) State and explain Kirchoff's voltage laws. 5
 (b) For the circuit shown below find the magnitude of current through an ammeter 'A'. Applying Kirchoff's voltage law. 5



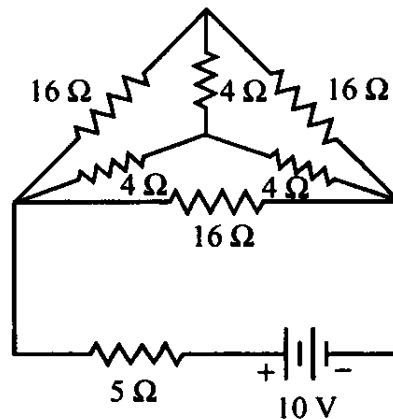11. For the network shown below determine :
 (i) Total circuit resistance (ii) Total circuit current
 Using Y – Δ transformation 10



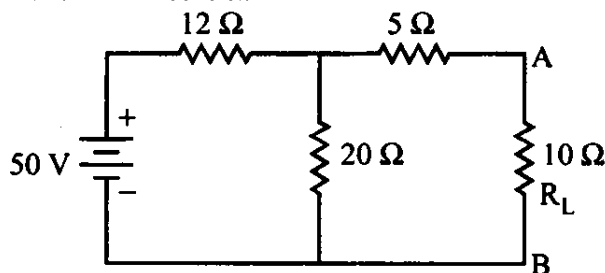12. (a) State the superposition theorem and explain. 5
 (b) Find the current through the load resistance 'RL' in the circuit shown below by applying Thevenin's theorem. 5



13. (a) (i) State the law of reluctance 5
 (ii) Define magnetizing force and mention its unit. 5
 (b) Compare magnetic circuit and electric circuit. 5

14. (a) Explain dynamically induced emf and statically induced emf. 6
(b) Define : (i) Self Inductance (ii) Mutual Inductance 4
15. (a) A coil of 50 cms length and 2 sq-cm area of cross section has 1500 turns on it. Find the inductance of the coil when the core is iron of $\mu_r = 800$ 5
(b) Define the following with respect to alternating quantity.
(i) Instantaneous value
(ii) Amplitude
(iii) Frequency
(iv) Cycle 5
16. (a) Define : (i) Average value (ii) Form factor
And write the equations. 5
(b) An alternating current is represented as $i = 0.707 \sin 400 t$.
Find : (i) RMS value (ii) Frequency (iii) Current
When, $t = 0.002$ secs after passing through zero in the +ve direction. 5
17. (a) Find the form factor of an alternating quantity current which has maximum value of 1.5 Amps. 5
(b) Derive an equation for power consumed in a pure resistive circuit. 5
18. (a) Explain RLC – series circuit with neat circuit diagram, waveform and vector diagram. 5
(b) A resistance 5Ω and an inductance of 0.1 Henry are connected in series across 200 V 50 Hz AC supply, find :
(i) Impedance (ii) current in the circuit 5
19. (a) Explain the condition for series resonance and draw the resonance curve. 5
(b) Three impedances $(5+j4)$ are connected in STAR across 440 V, 3 ϕ 50 Hz AC supply. Calculate :
(i) Phase current
(ii) Line current
(iii) Power factor
(iv) Power consumed 5
-