

1756**Code : 15EE21T**Register
Number

--	--	--	--	--	--	--

II Semester Diploma Examination, April/May-2018**ELECTRICAL CIRCUITS****Time : 3 Hours]****[Max. Marks : 100**

- Note :** (i) Answer any **six** questions from Part – A. Each question carries **5** marks.
(ii) Answer any **seven** questions from Part – B. Each question carries **10** marks.


PART – A

1. Explain closed circuit, open circuit, short circuit with neat circuit diagram. **5**
2. Define :
 - (i) Bilateral circuit
 - (ii) Unilateral circuit **5**
3. Define and mention SI units for the followings : **5**
 - (i) Absolute permeability
 - (ii) Relative permeability
4. List the difference between electric circuit and magnetic circuit. **5**
5. State and explain Fleming's right hand rule. **5**
6. Define power and power factor in AC circuit. **5**


7. Define : 5
- RMS value of alternating current.
 - Average – value of an alternating current and write their equations.
8. Derive an equation for power in pure resistive circuit. 5
9. List advantages of 3-phase system over 1 – ϕ system. 5

PART – B

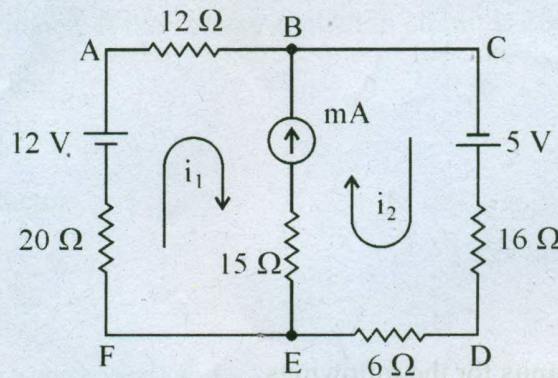
10. (a) Define the followings : 4
- Linear circuit
 - Non-linear circuit
- (b) By applying Kirchhoff's law find the current through the milliammeter connected to the circuit below. 6



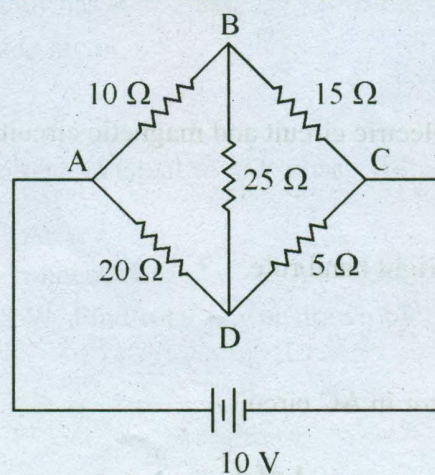11. (a) Derive an expression for star – delta transformation. 5
- (b) Using star-delta transformation find the total current for the circuit given below : 5



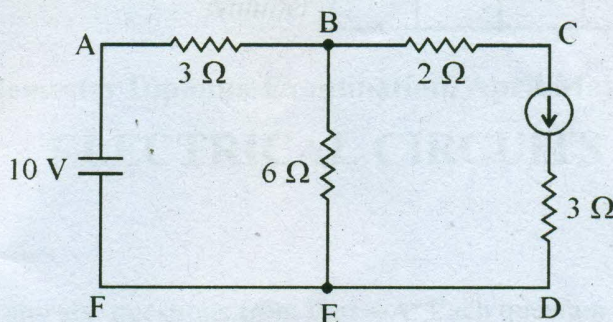12. (a) State and explain maximum power transfer theorem. 5
 (b) Prove Reciprocity theorem for the circuit given below : 5



13. (a) Define the following : 4
 (i) Magnetic flux (ϕ)
 (ii) Flux density (B)
 (b) An air cored toroidal coil has 3000 turns and carries a current of 0.1 A. The cross sectional area of the coil is 4 cm^2 and length of magnetic circuit is 15 cm. Determine the magnetic field strength, flux density and total flux in the coil. 6
14. (a) State and explain : 6
 (i) Fleming's right hand rule
 (ii) Cork's screw rule
 (b) Define self inductance and co-efficient of self inductance of a coil with units. 4
15. (a) Draw sinusoidal waveform and mark the following : 5
 (i) Instantaneous value
 (ii) Amplitude
 (iii) Cycle
 (iv) Frequency
 (v) Time period
 (b) A sinusoidal alternating current is represented by $i = 30 \sin 30 t$. 5
 Find :
 (i) maximum value
 (ii) current when $t = 0.002 \text{ sec}$ passing through zero in the direction
 (iii) RMS value of current

[Turn over

16. (a) Derive an expression for instantaneous value of alternating voltage and current. 5
- (b) If $I_1 = 2 + i3$ 5
 $I_2 = 5 + i6$
Perform
(i) $I_1 + I_2$
(ii) $I_1 - I_2$
(iii) $I_1 \times I_2$
(iv) $\frac{I_1}{I_2}$
17. (a) With diagram explain pure resistive circuit. 5
- (b) An AC series circuit consisting of 10Ω resistance, 0.05 h inductance and $100 \mu\text{F}$ capacitance. If the voltage applied to circuit is $200 \text{ V } 60 \text{ Hz}$, find : 5
(i) Impedance
(ii) Current
(iii) Power factor
18. (a) Define : 5
(i) Inductive reactance (X_L)
(ii) Capacitive reactance (X_C)
- (b) A series RLC circuit has $R = 50 \Omega$, $L = 50 \mu\text{h}$ and $c = 1000 \text{ pf}$, find resonant frequency (f_r) and Q factor. 5
19. (a) Prove that line voltage is equal to $\sqrt{3}$ phase voltage in a 3 - ϕ star connected system. 5
- (b) Two wattmeters connected to 3 - ϕ AC line to measure power and reads 6717 W and 2538 W . Find total power drawn by the balanced load and power factor. 5